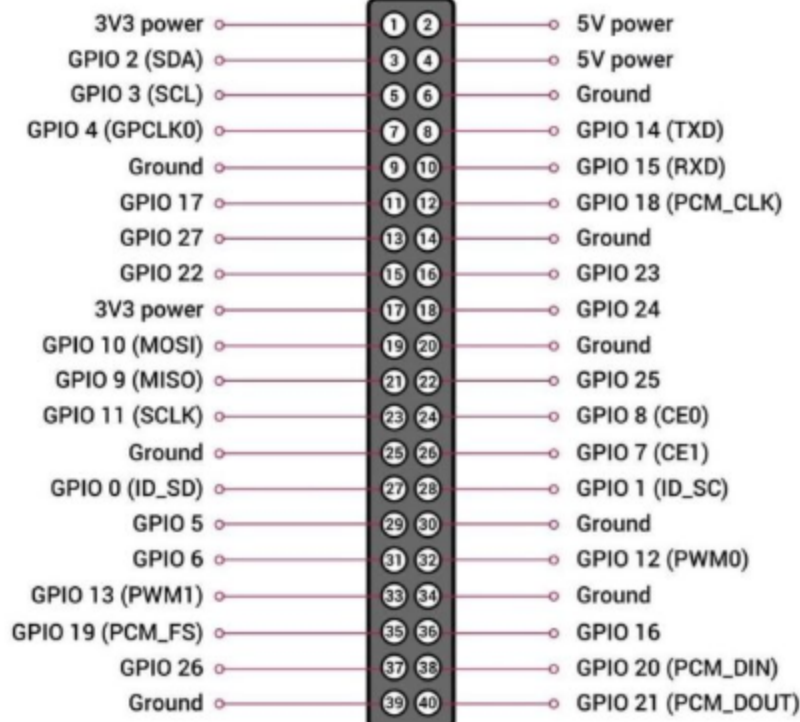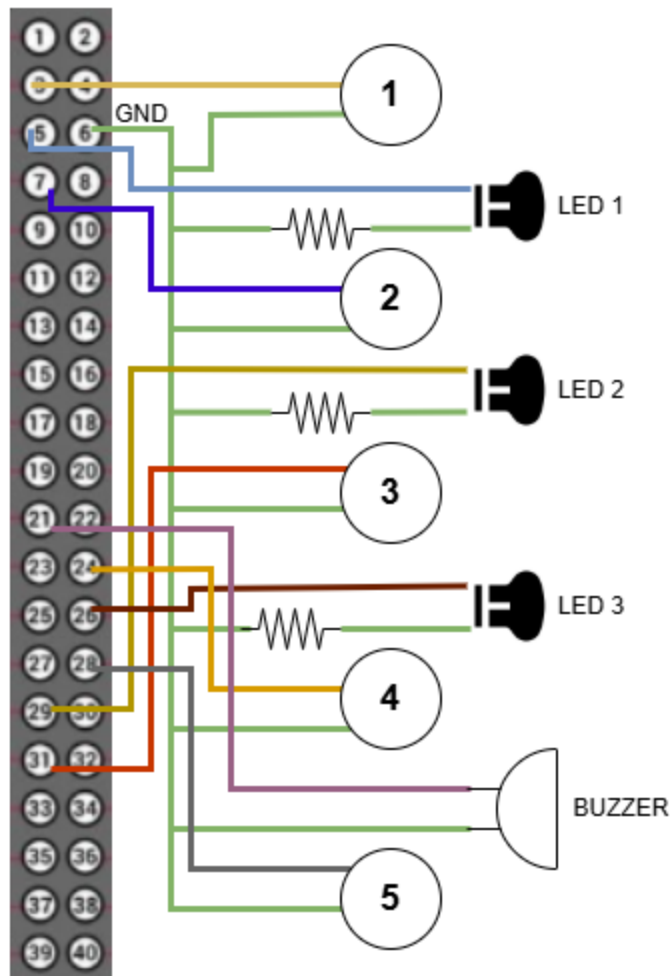Raspberry Pi 5

Raspberry Pi 5 Pin Diagram

Button 1 : GPIO pin -> 2 and GND
Button 2 : GPIO pin -> 4 and GND
Button 3 : GPIO pin -> 6 and GND
Button 4 : GPIO pin -> 8 and GND
Button 5 : GPIO pin -> 1 and GND

LED 1 : GPIO pin -> 3 and GND
LED 2 : GPIO pin -> 5 and GND
LED 3 : GPIO pin -> 7 and GND

Buzzer : GPIO pin -> 9 and GND